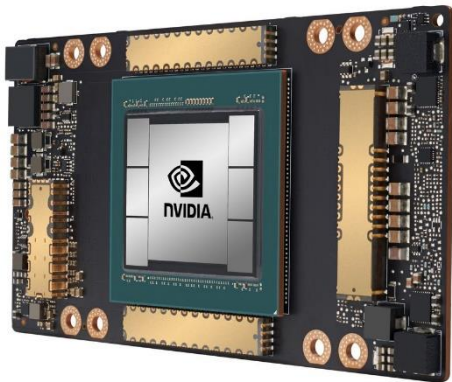



# CSCB58: Computer Organization



Prof. Gennady Pekhimenko

University of Toronto

Fall 2020

 

*The content of this lecture is adapted from the lectures of  
Larry Zheng and Steve Engels*


# **CSCB58 Week 7**

# Circuit Timing

# Timing

- So far we have been worrying whether a circuit is correct.
- Now let's think about how to make a circuit fast.
- Key concept: latency
  - propagation delay
  - contamination delay


# Delay Example

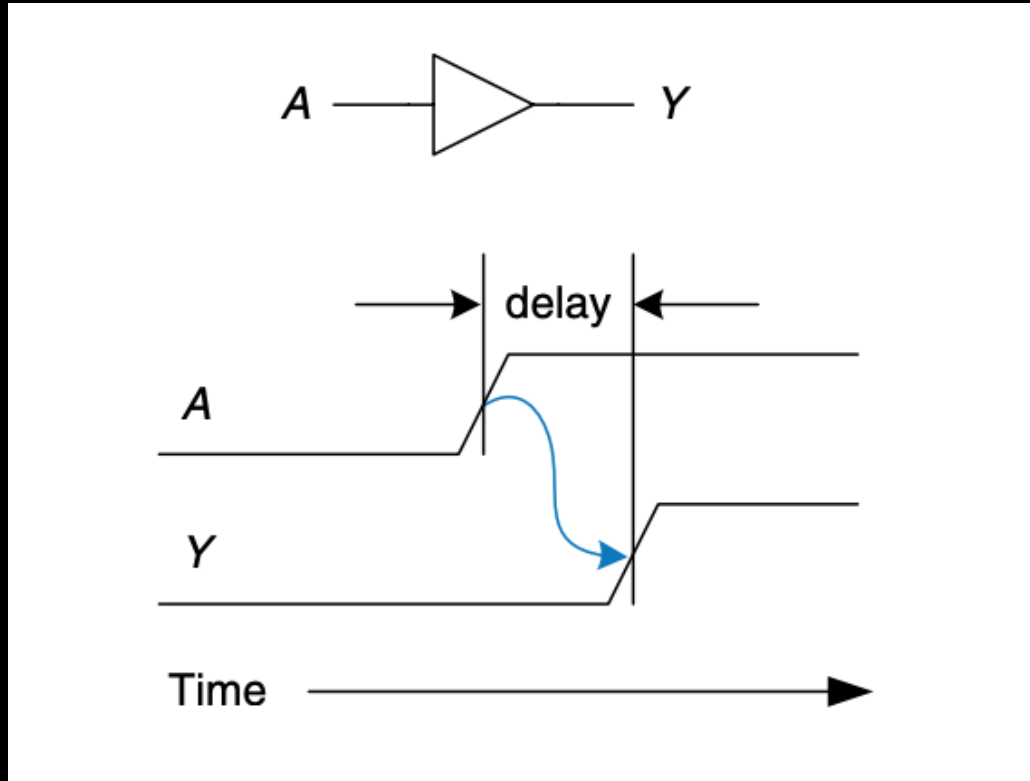


- We measure the interval between the two “50% points” of the changing signals
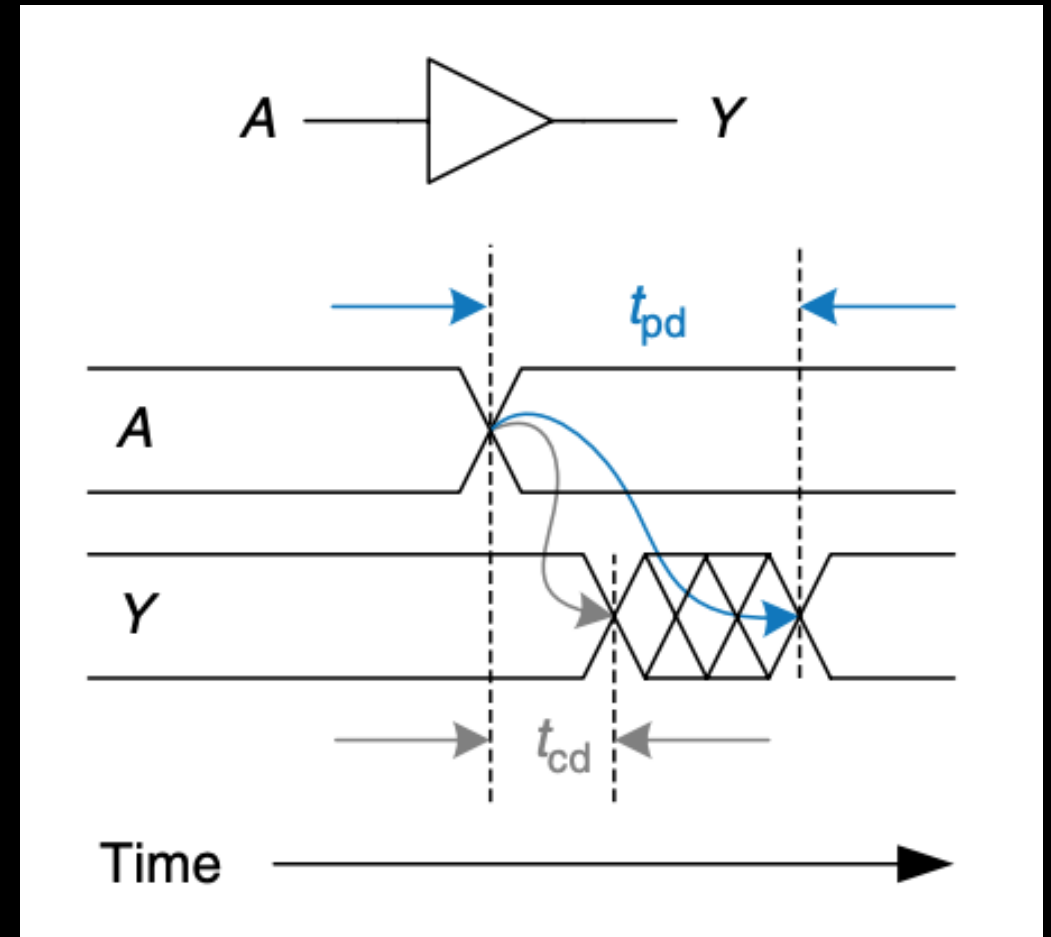
# Propagation & Contamination Delay

- **Propagation delay:** the maximum time from when an input changes until the output or outputs reach their final value.
- **Contamination delay:** the minimum time from when an input changes until any output starts to change its value.




 Given a circuit diagram,  
calculate its propagation delay  
and contamination delay


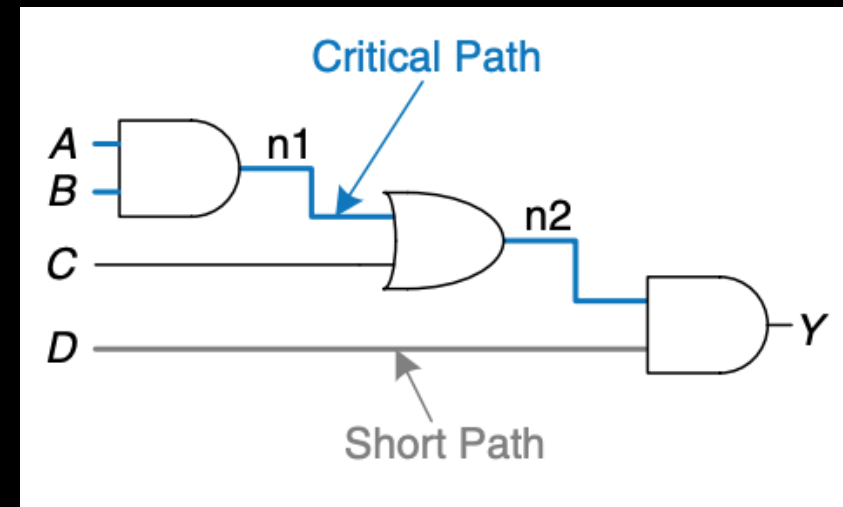
# Need to know

- The propagation and contamination delay of each logic gate used




Gate	t <sub>pd</sub> (propagation)	t <sub>cd</sub> (contamination)
2-input AND	100 picoseconds	60 picoseconds
2-input OR	120 picoseconds	40 picoseconds


 
# Calculate Propagation Delay


- Find the **critical path** (path with the largest number of gates)
- then sum up the **propagation** delay of all the gates on the critical path
- $100 + 120 + 100 = 320$  picoseconds



Gate	t <sub>pd</sub>	t <sub>cd</sub>
2-input AND	100 ps	60 ps
2-input OR	120 ps	40 ps
 
# Calculate Contamination Delay


- Find the **short path** (path with the smallest number of gates)
- then sum up the **contamination** delay of all the gates on the short path
- 60 picoseconds



Gate	t <sub>pd</sub>	t <sub>cd</sub>
2-input AND	100 ps	60 ps
2-input OR	120 ps	40 ps

Knowing how to calculate delays allows us to design circuits that are fast.

# Quick intro: Tri-state buffer

 


WE	A	Y
0	x	z
1	0	0
1	1	1



WE = 1



WE = 0


 


# Example: design fast circuit

  


two different  
4-1 muxes

# Example: design fast circuit

  


 - We care about the **propagation** delays of the two circuits.
  - it tells us “how soon I can get the answer”
- More specifically, we care about the D-to-Y delay and S-to-Y delay because D and S may arrive at different time.



Gate	$t_{pd}$ (ps)
NOT	30
2-input AND	60
3-input AND	80
4-input OR	90
tristate (A to Y)	50
tristate (enable to Y)	35

 - D-to-Y propagation delay:
- $2 \times \text{TRISTATE\_AY} = 100$
- S-to-Y propagation delay
- $\text{TRISTATE\_ENY} + \text{TRISTATE\_AY}$
- $= 35 + 50 = 85$





Gate	$t_{pd}$ (ps)
NOT	30
2-input AND	60
3-input AND	80
4-input OR	90
tristate (A to Y)	50
tristate (enable to Y)	35

- D-to-Y propagation delay:
- $\text{TRISTATE\_AY} = 50$
- S-to-Y propagation delay
- $\text{NOT} + \text{AND2} + \text{TRISTATE\_ENY}$
- $= 30 + 60 + 35 = 125$



  
# Analysis result

- Circuit 1 propagation:
  - D-to-Y: 100 ps
  - S-to-Y: 85 ps
- Circuit 2 propagation
  - D-to-Y: 50 ps
  - S-to-Y: 125 ps
- Which circuit is faster?
  - What if D and S arrive at the same time?
  - What if D arrives earlier than S?
  - What if S arrives earlier than D?


 
# Delays: the lower/higher, the better?

- Propagation delay, typically, should be upper-bounded.
  - shorter propagation means getting answer faster
  - How to make it lower?
  - shorten the critical path
- Contamination delay, typically, should be lower-bounded
  - want to reliably sample the value before change.
  - How to make it longer?
  - add **buffers** to the short path






New Topic:  
**Processor  
Components**




Using what we have learned so far  
(combinational logic, devices, sequential  
circuits, FSMs), **how do we build a processor?**

# The Final Destination

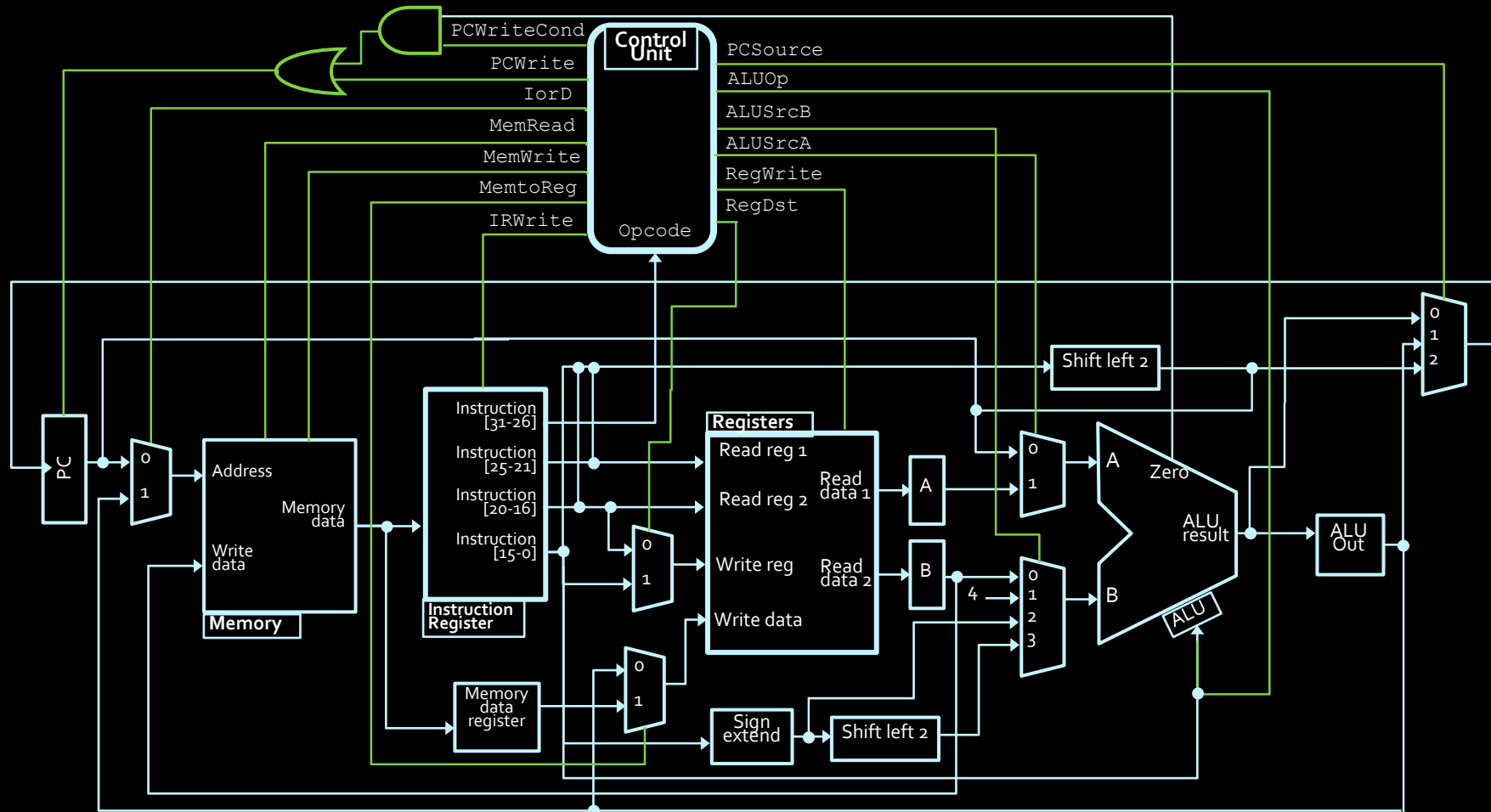


# Deconstructing processors

- Simpler at a high level:

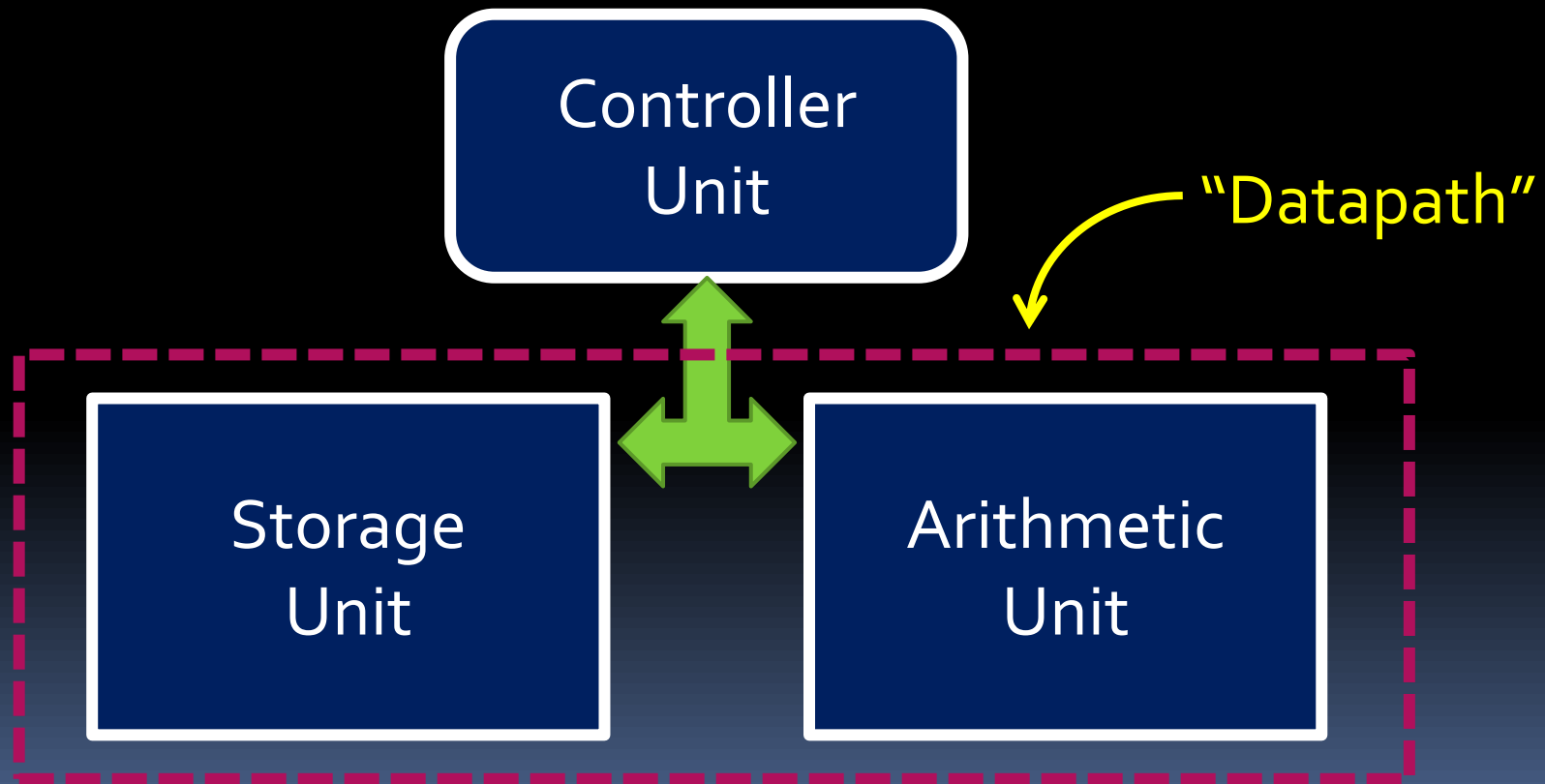




# Datapath vs. Control

- **Datapath:** where all data computations take place.
    - Often a diagram version of real wired connections.
  - **Control unit:** orchestrates the actions that take place in the datapath.
    - The control unit is a big finite-state machine that instructs the datapath to perform all appropriate actions.
- 




# Datapath example

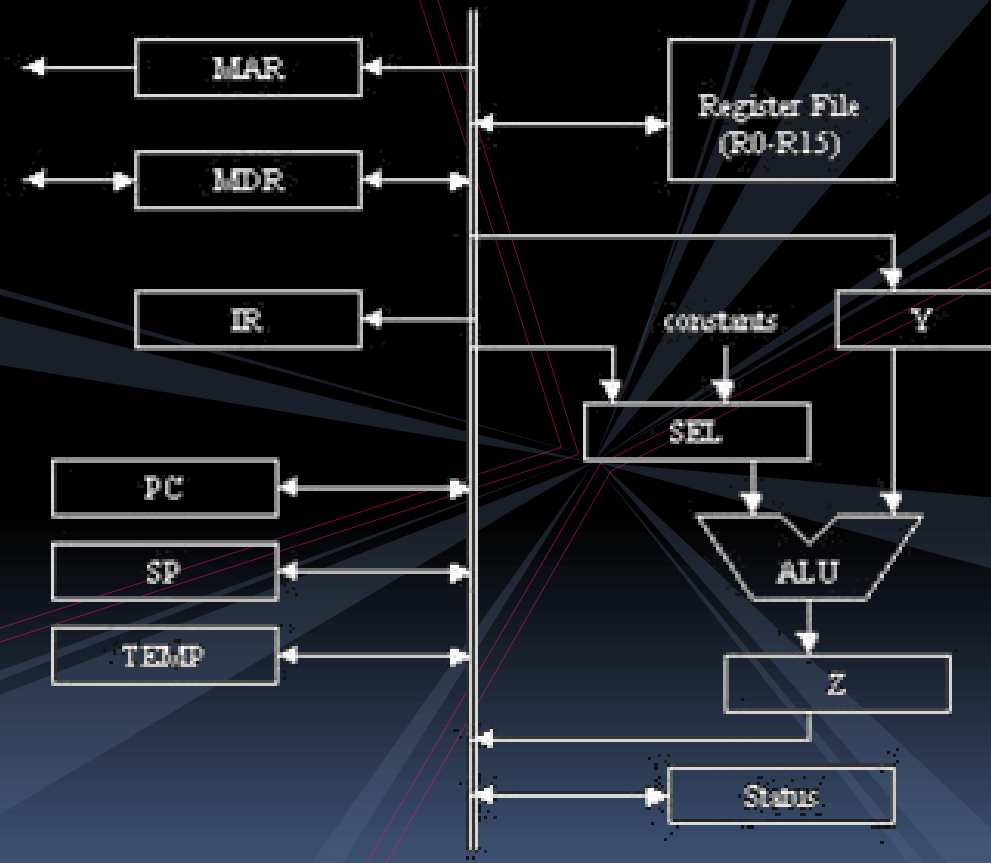

# Example: Calculate $x^2 + 2x$


- Assume that you have access to a value from an external source. How would you calculate  $x^2 + 2x$  with components you've seen so far?
- Components needed:
  - **ALU** (to add, subtract and multiply values)
  - **Multiplexers** (to determine what the inputs should be to the ALU)
  - **Registers** (to hold values used in the calculation)

# Example schematic

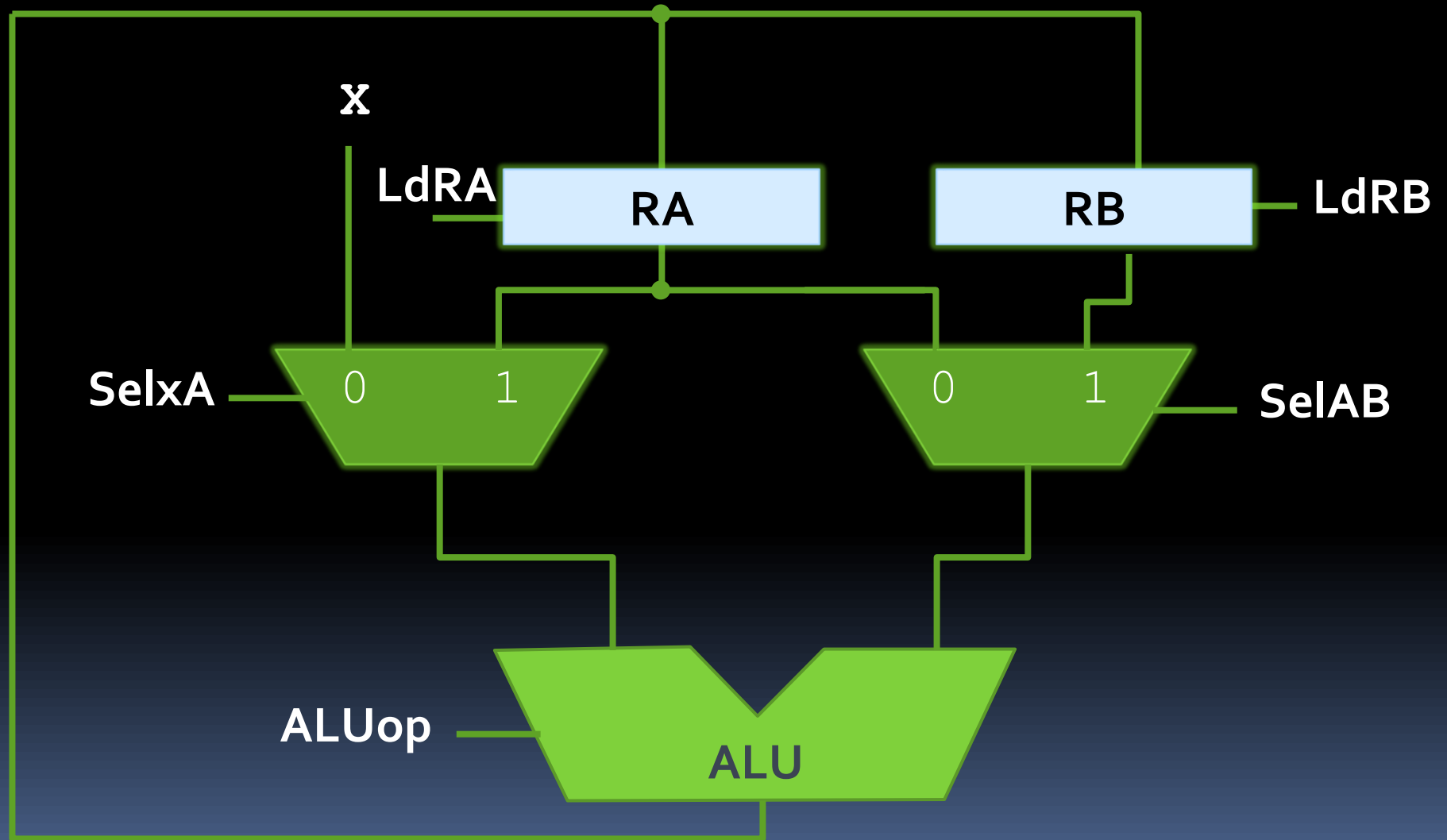
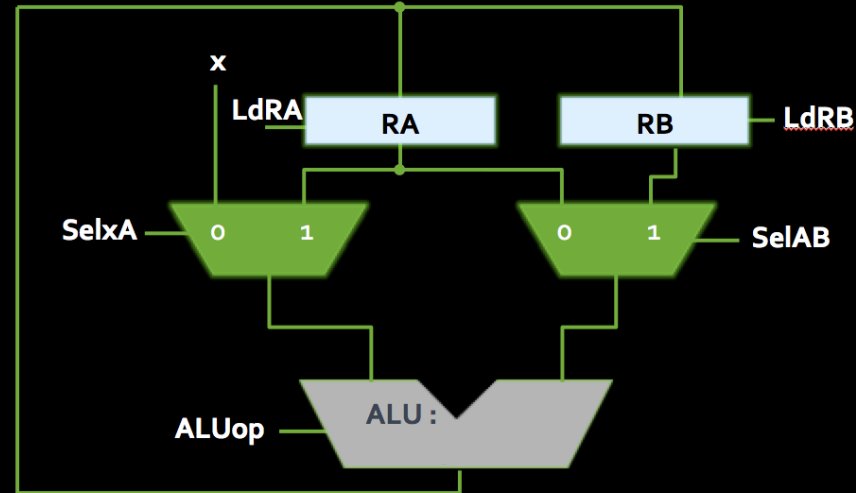
# Making the calculation

- Steps for  $x^2 + 2x$ :
  - Load X into RA & RB
    - Store result in RA
  - Multiply RA & RB
    - Store result in RA
  - Add X to RA
    - Store result in RA
  - Add X to RA again
    - ALU output is  $x^2 + 2x$ .
  
- How do we make this happen?



# Making the calculation

## High-level Steps

- Load X into RA & RB
- Multiply RA & RB
  - Store result in RA
- Add X to RA
  - Store result in RA
- Add X to RA again
  - ALU output is  $x^2 + 2x$ .

## Control Signals

- SelxA = 0, ALUop = A,  
LdRA = 1, LdRB = 1
- SelxA = 1, SelAB = 1,  
ALUop = Multiply, LdRA = 1
- SelxA = 0, SelAB = 0,  
ALUop = Add, LdRA = 1
- SelxA = 0, SelAB = 0,  
ALUop = Add


- **Who sends these signals?**



# Control Unit


- Basically, a giant Finite State Machine
  - Synchronized to system-wide signals (**clock**, **resetsn**)
- Outputs the **datapath control signals**
  - **SelxA, SelAB** => control mux outputs (ALU inputs)
  - **ALUop** => controls ALU operation
  - **LdRA, LdRB** => controls loading for registers RA, RB
- Some architectures also output a **done** signal, when the computation is complete
  - Yet another output; not shown in our datapaths

# Datapath + Control

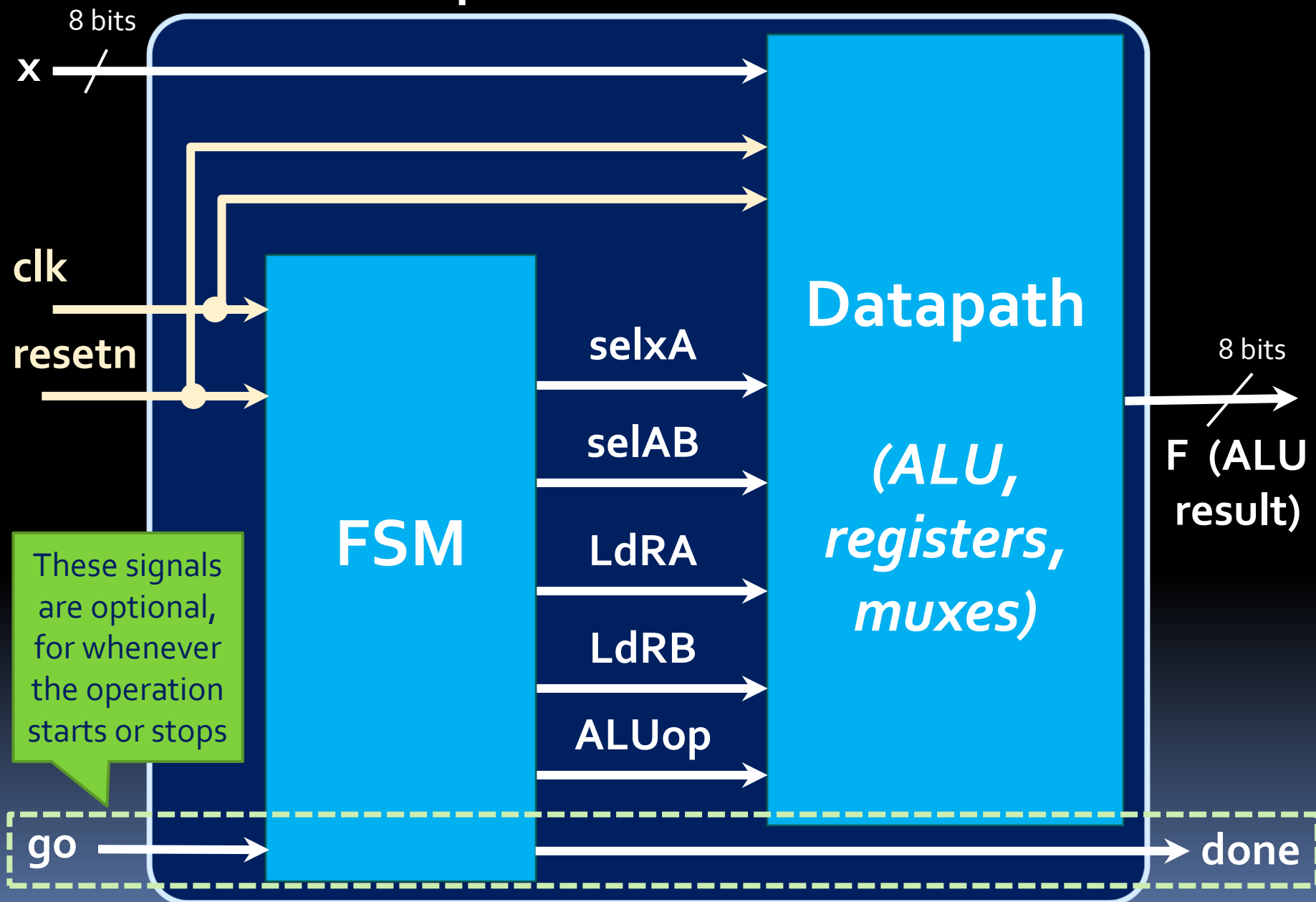

 
# Microprocessors

- So far, we've been talking about making devices, such as adders, counters and registers.
- The ultimate goal is to make a **microprocessor**, which is a digital device that processes input, can store values and produces output, according to a set of on-board instructions.






# The Final Destination

 

 
# Deconstructing processors

- Processors aren't so bad when you consider them piece by piece:


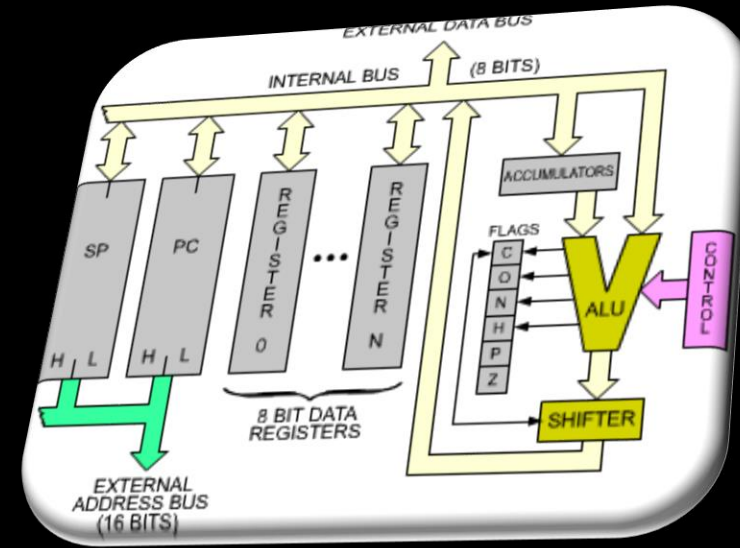
# Microprocessors

- These devices are a combination of the units that we've discussed so far:
  - **Registers** to store values.
  - **Adders** and **shifters** to process data.
  - **Finite state machines** to control the process.
- Microprocessors are the basis of all computing since the 1970's, and can be found in nearly every sort of electronics.




# The “Arithmetic Thing”

aka: the Arithmetic Logic Unit (ALU)




# We are here

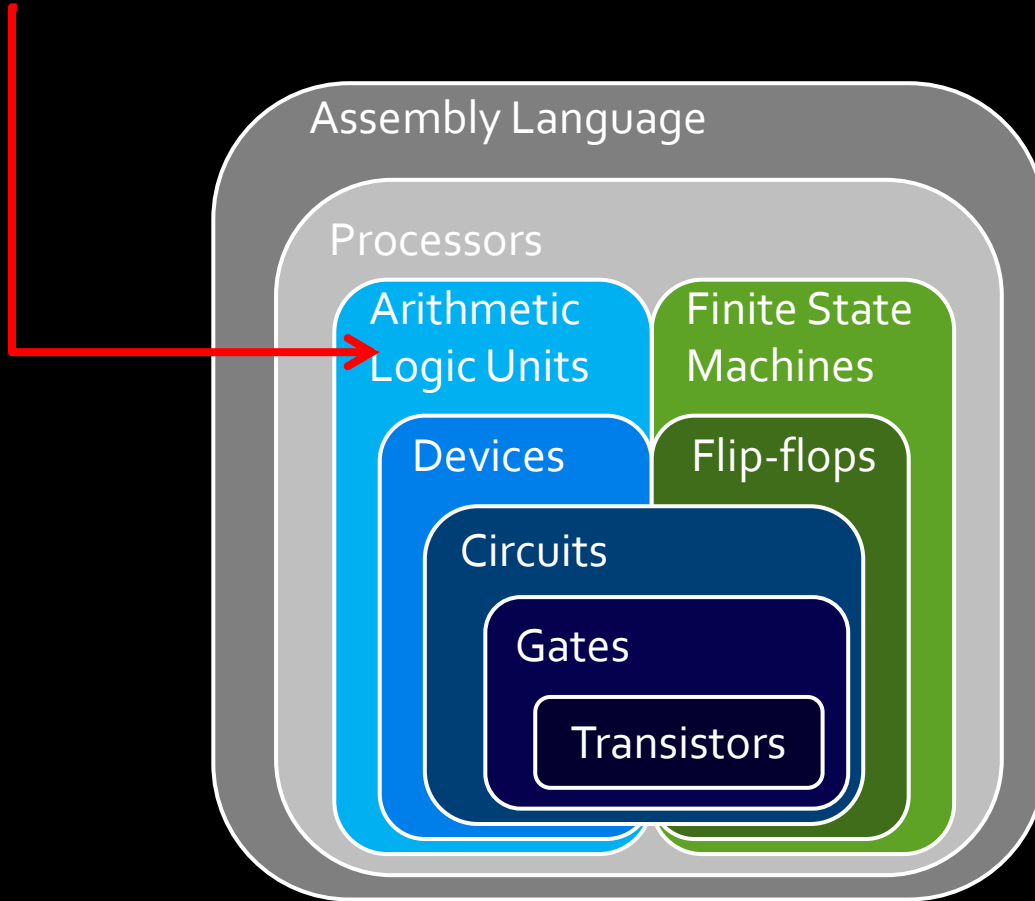

 
# Arithmetic Logic Unit

- The first microprocessor applications were calculators.
  - Recall the unit on adders and subtractors.
  - These are part of a larger structure called the **arithmetic logic unit** (ALU).
- This larger structure is responsible for the processing of all data values in a basic CPU.



 
# ALU inputs

- The ALU performs all of the arithmetic operations covered in this course so far, and logical operations as well (AND, OR, NOT, etc.)
  - A and B are the operands
  - The select bits (S) indicate which operation is being performed (S<sub>2</sub> is a mode select bit, indicating whether the ALU is in arithmetic or logic mode).
  - The carry bit  $C_{in}$  is used in operations such as incrementing an input value or the overall result.


 
# ALU outputs


- In addition to the input signals, there are output signals V, C, N & Z which indicate special conditions in the arithmetic result:
  - **V**: overflow condition
    - The result of the operation could not be stored in the  $n$  bits of  $G$ , meaning that the result is incorrect.
  - **C**: carry-out bit
  - **N**: Negative indicator
  - **Z**: Zero-condition indicator





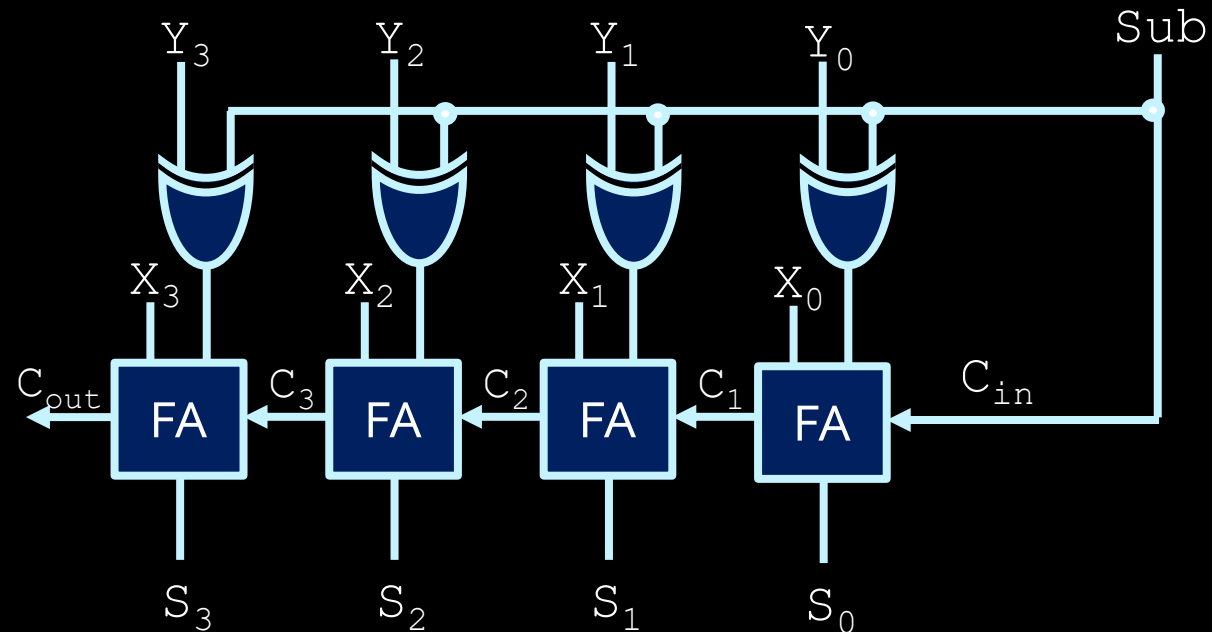
# The “A” of ALU

- To understand how the ALU does all of these operations, let's start with the arithmetic side.
- Fundamentally, this side is made of an adder / subtractor unit, which we've seen already:



 
# ALU block diagram

- In addition to data inputs and outputs, this circuit also has:
  - outputs indicating the different conditions,
  - inputs specifying the operation to perform (similar to `Sub`).




# Arithmetic components

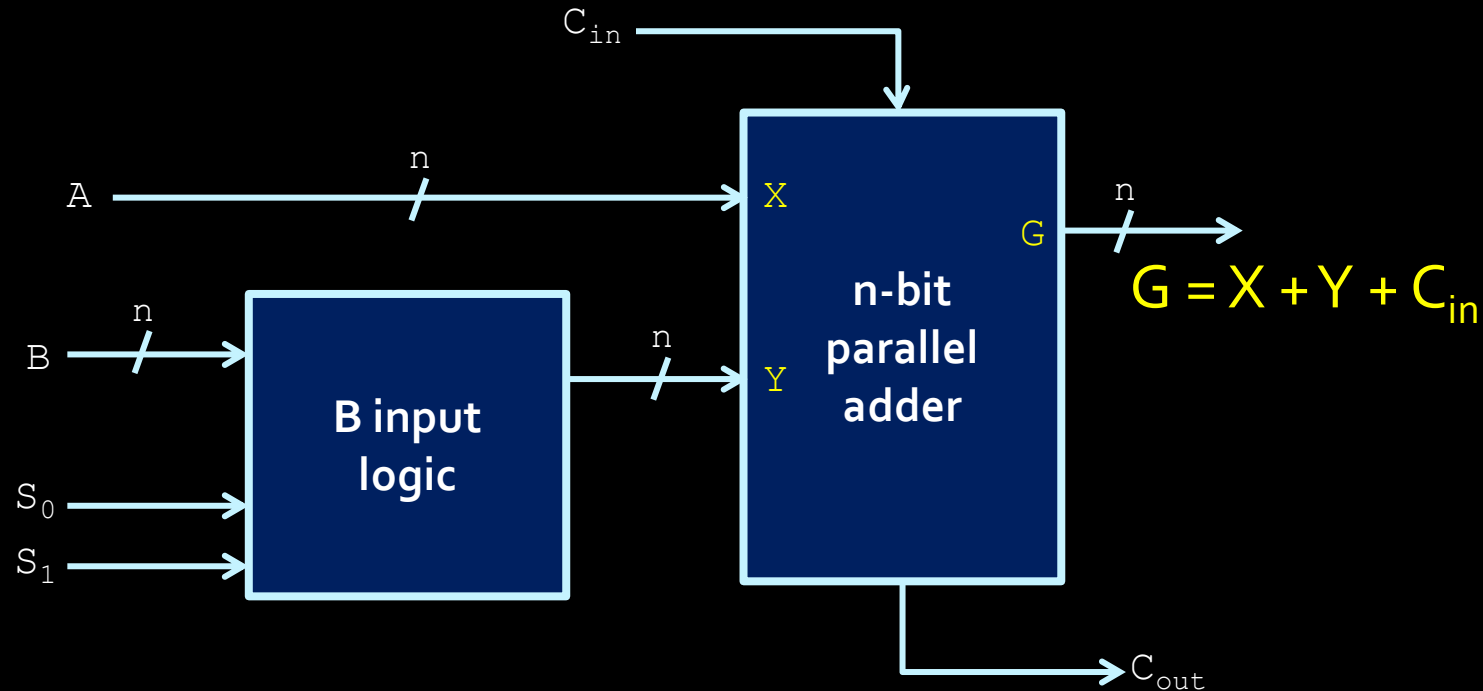

- In addition to addition and subtraction, many more operations can be performed by manipulating what is added to input  $B$ , as shown in the diagram above.

# Arithmetic operations

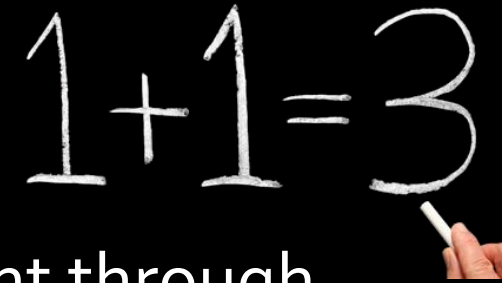

A hand-drawn equation  $1+1=3$  written in white chalk on a black background. A hand is visible at the bottom right, holding a piece of white chalk and pointing towards the number 3.

- If the input logic circuit on the left sends B straight through to the adder, result is  $G = A+B$
  - What if B was replaced by all ones instead?
    - Result of addition operation:  $G = A-1$
  - What if B was replaced by  $\overline{B}$ ?
    - Result of addition operation:  $G = A-B-1$
  - And what if B was replaced by all zeroes?
    - Result is:  $G = A$ . (Not interesting, but useful!)
- Instead of a Sub signal, the operation you want is signaled using the select bits  $S_0$  &  $S_1$ .

# Operation selection

Select bits		Y input	Result	Operation
$S_1$	$S_0$			
0	0	All 0s	$G = A$	Transfer
0	1	B	$G = A+B$	Addition
1	0	$\bar{B}$	$G = A+\bar{B}$	Subtraction - 1
1	1	All 1s	$G = A-1$	Decrement

- This is a good start! But something is missing...
- What about the carry bit?


# Full operation selection

Select		Input	Operation	
$S_1$	$S_0$	Y	$C_{in}=0$	$C_{in}=1$
0	0	All 0s	$G = A$ (transfer)	$G = A+1$ (increment)
0	1	B	$G = A+B$ (add)	$G = A+B+1$
1	0	$\bar{B}$	$G = A+\bar{B}$	$G = A+\bar{B}+1$ (subtract)
1	1	All 1s	$G = A-1$ (decrement)	$G = A$ (transfer)


- Based on the values on the select bits and the carry bit, we can perform any number of basic arithmetic operations by manipulating what value is added to  $A$ .
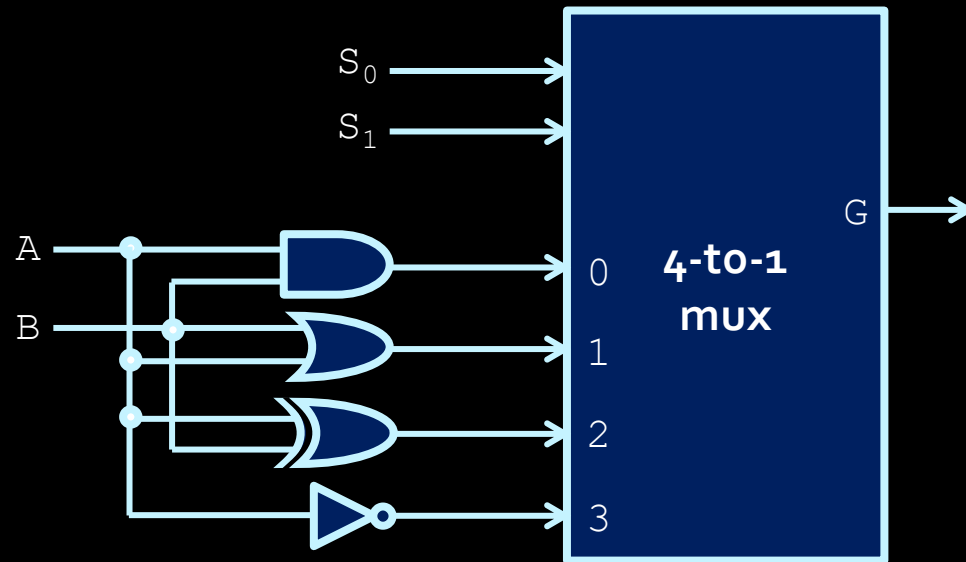
# The “L” of ALU

- We also want a circuit that can perform **logical operations**, in addition to arithmetic ones.
- How do we tell which operation to perform?
  - Another select bit!
- If  $S_2 = 1$ , then logic circuit block is activated.
- Multiplexer is used to determine which block (logical or arithmetic) goes to the output.



# Single ALU Stage

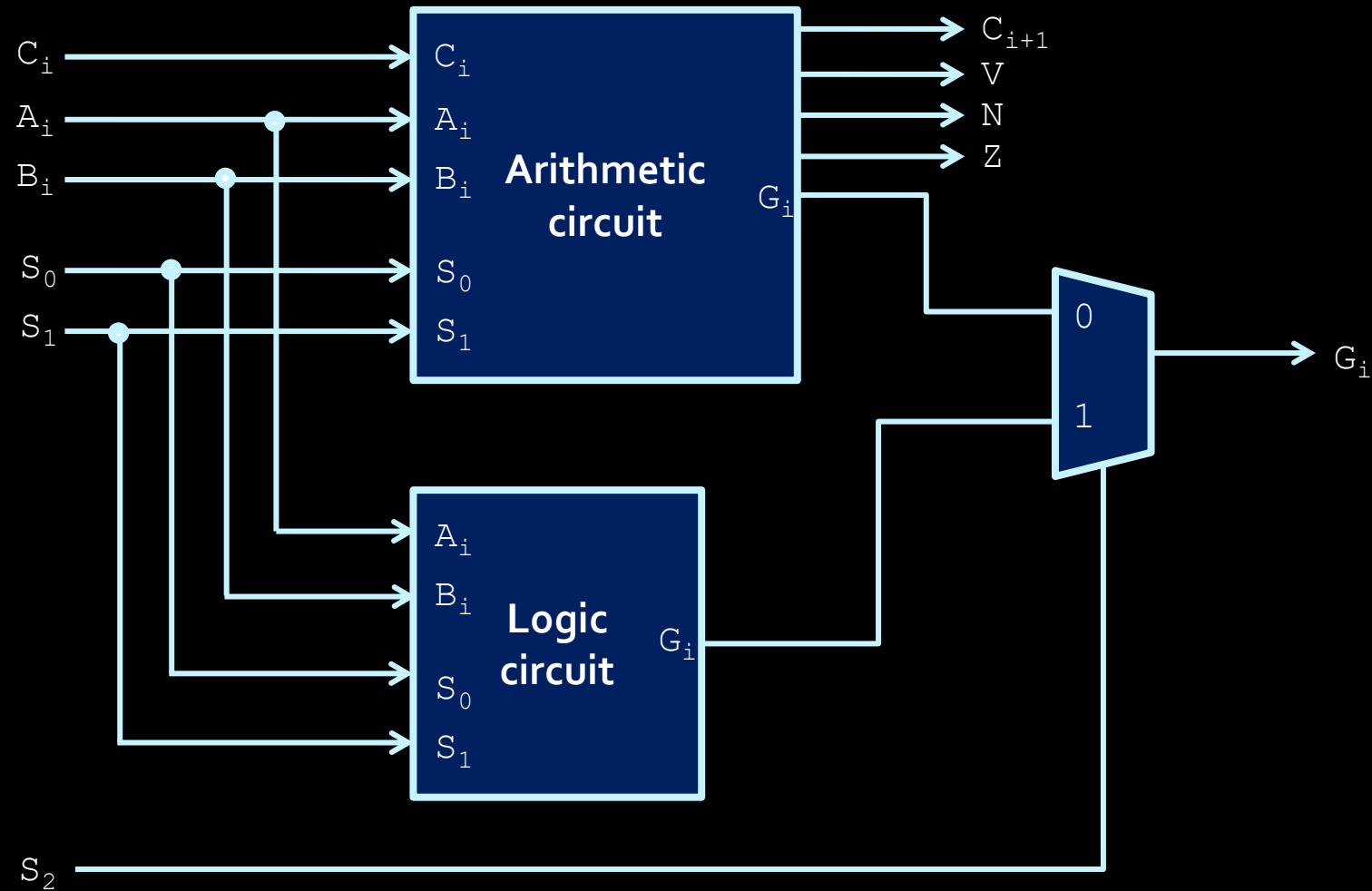




# Multiplication

# What about multiplication?

- Multiplication (and division) operations are always more complicated than other arithmetic (addition, subtraction) or logical (AND, OR) operations.
- Three major ways that multiplication can be implemented in circuitry:
  - Layered rows of adder units.
  - An adder/shifter circuit
  - Booth's Algorithm

 
# Multiplication

- Multiplier circuits can be constructed as an array of adder circuits.
- This can get a little expensive as the size of the operands grows.
- Is there an alternative to this circuit?




# Multiplication

- Revisiting grade 3 math...

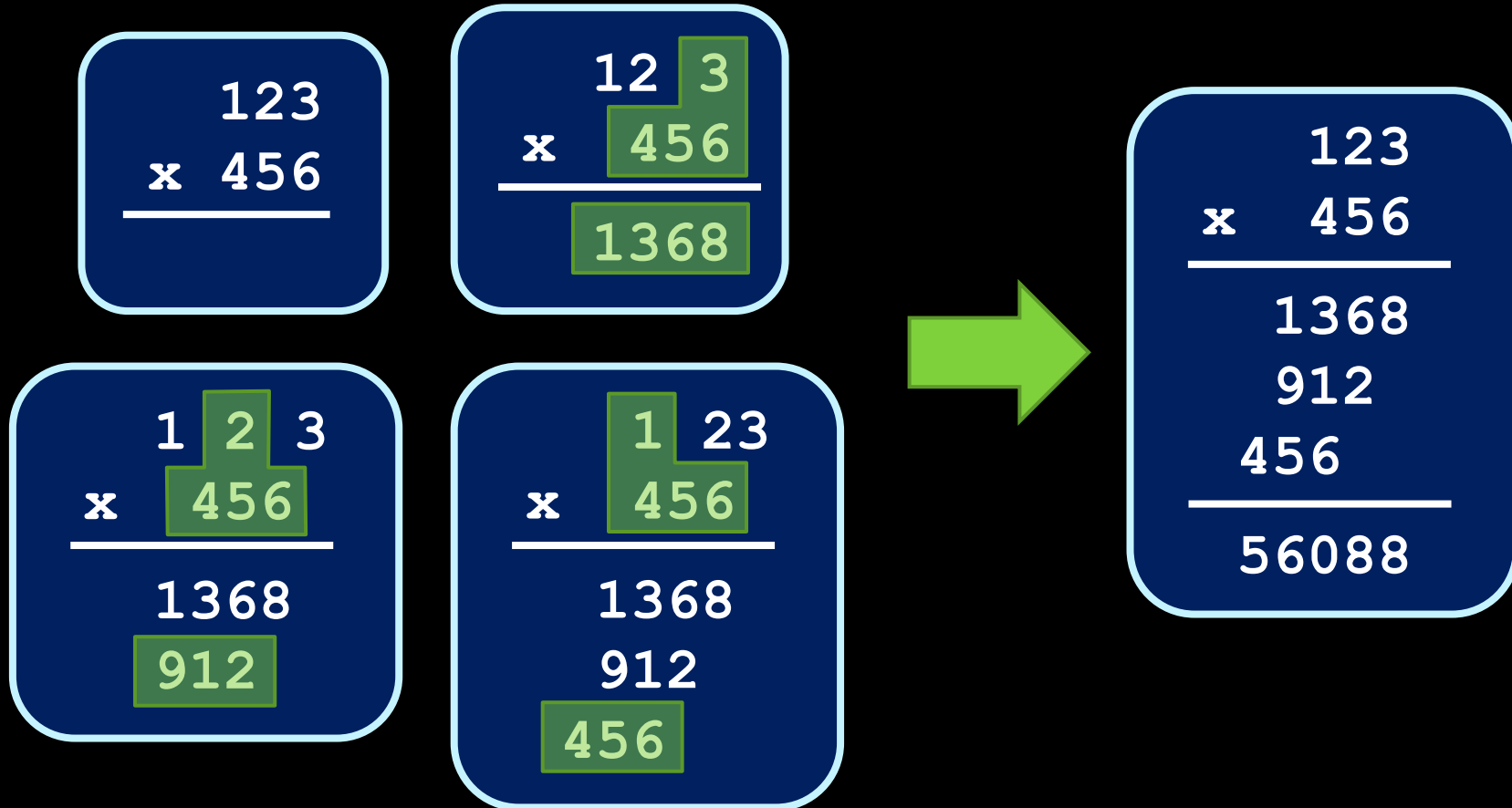

# Multiplication

- And now, in binary...

 



# Observations

- Calculation flow
  - Multiply by 1 bit of multiplier
  - Add to sum and shift sum
  - Shift multiplier by 1 bit
  - Repeat the above
- What is “multiply by 1 bit of binary”?
  - $10101 \times 1$  ?
  - $10101 \times 0$  ?
  - It's an **AND**!

$$\begin{array}{r} 101 \\ \times 110 \\ \hline 110 \\ 000 \\ 110 \\ \hline 11110 \end{array}$$
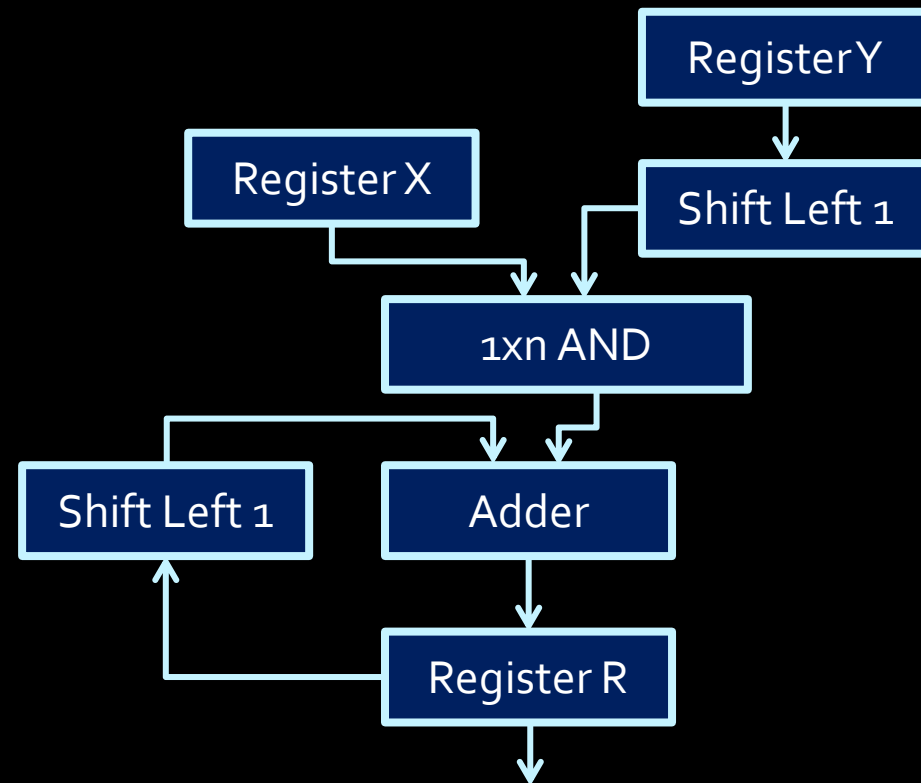 
# Accumulator circuits

- What if you could perform each stage of the multiplication operation, one after the other?
  - This circuit would only need a single row of adders and a couple of shift registers.



# Make it more efficient

Think about  $258 \times 9999$

- Multiply by 9, add to sum, shift, multiply by 9, add to sum, shift, multiple by 9, add to sum, shift, multiply by 9, add to sum.
- $258 \times 9999 = 258 \times (10000 - 1) = 258 \times 10000 - 258$
- Just shift 258, becomes 2580000, then do  $2580000 - 258$
- More efficient!




# Efficient Multiplication: Booth's Algorithm

- Take advantage of circuits where **shifting is cheaper** than adding, or where space is at a premium.
  - when multiplying by certain values (e.g. 99), it can be easier to think of this operation as a difference between two products.
- Consider the shortcut method when multiplying a given decimal value  $X$  by 9999:
  - $X * 9999 = X * 10000 - X * 1$
- Now consider the equivalent problem in binary:
  - $X * 001111 = X * 010000 - X * 1$
- More details: [https://en.wikipedia.org/wiki/Booth%27s\\_multiplication\\_algorithm](https://en.wikipedia.org/wiki/Booth%27s_multiplication_algorithm)

# Reflections on multiplication


- Multiplication isn't as common an operation as addition or subtraction, but occurs enough that its implementation is handled in the hardware.
- Most common multiplication and division operations are powers of 2. For this, we do shifting instead of using the multiplier circuit.
  - e.g., in your code, do `x << 3`, instead of `x * 8`

# A Barrel Shifter unit

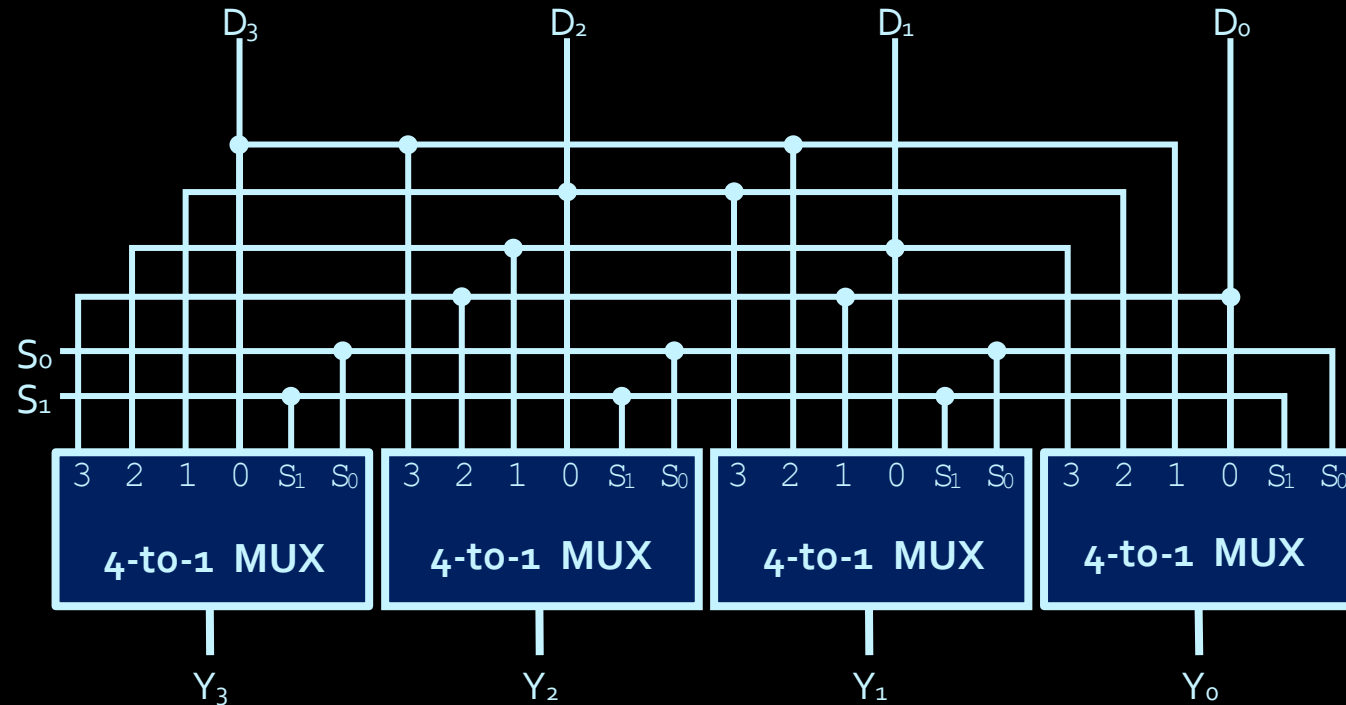


- This barrel shifter **shifts and rotates**  $D$  to the left by  $S$  bits.
  - If  $S_1S_0$  is 01  $\Rightarrow Y = D_2D_1D_0D_3$
  - If  $S_1S_0$  is 11  $\Rightarrow Y = D_0D_3D_2D_1$
- This is a **purely combinational circuit**, unlike the shift registers in the lab.


# Expanding our view

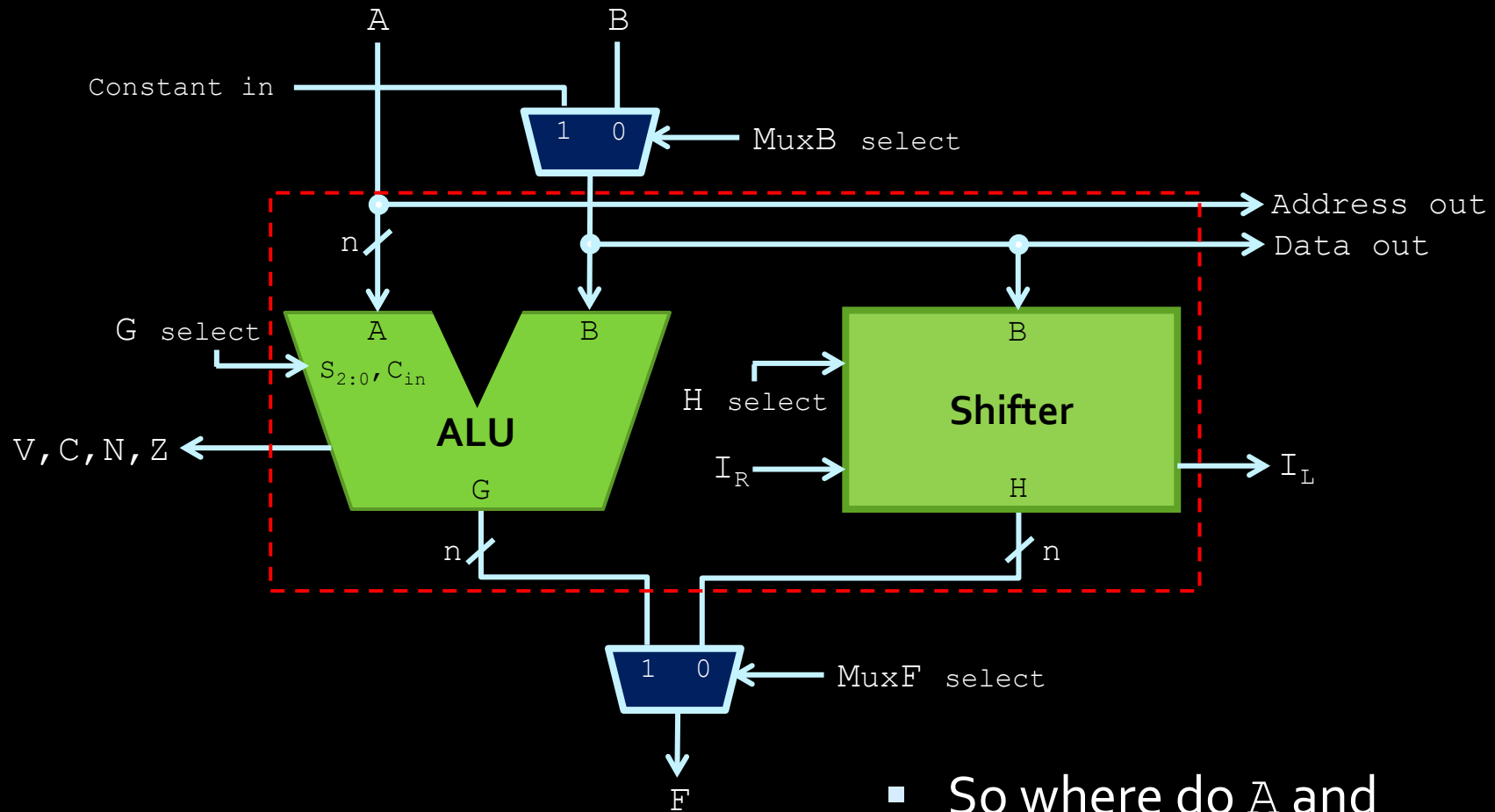

 - So where do  $\bar{A}$  and B come from?




# CSCB58: Computer Organization

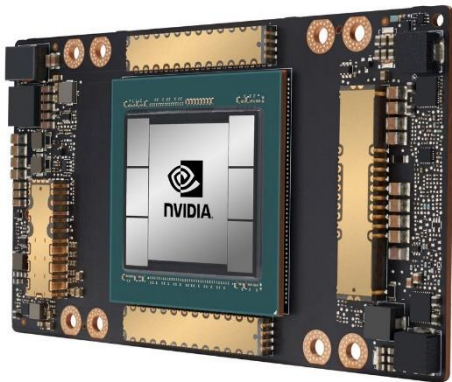

Prof. Gennady Pekhimenko

University of Toronto


Fall 2020

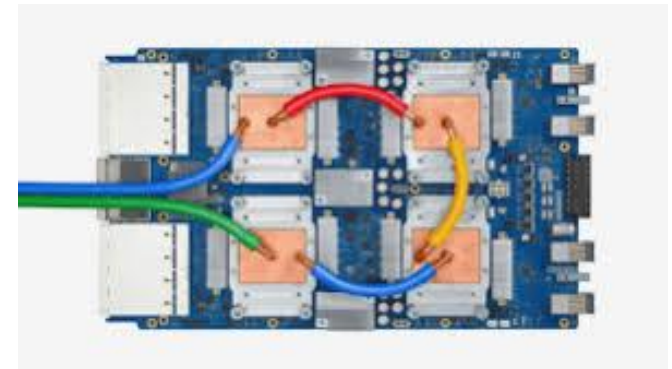

*The content of this lecture is adapted from the lectures of  
Larry Zheng and Steve Engels*




# Booth's Algorithm

- This idea is triggered on cases where two neighboring digits in an operand are different.
    - If digits at  $i$  and  $i-1$  are 0 and 1, the multiplicand is added to the result at position  $i$ .
    - If digits at  $i$  and  $i-1$  are 1 and 0, the multiplicand is subtracted from the result at position  $i$ .
  - The result is always a value whose size is the sum of the sizes of the two multiplicands.
- 

# Booth's Algorithm

- Example:

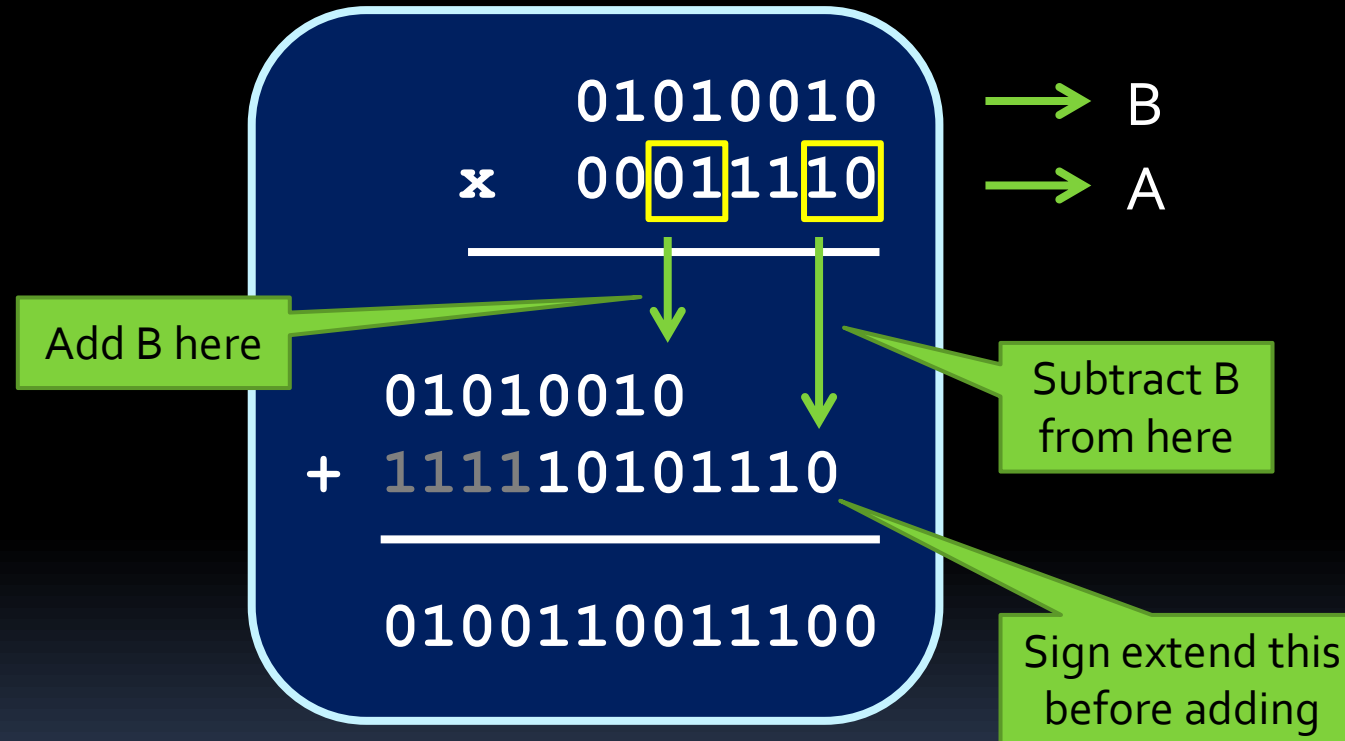



# Booth's Algorithm

- We need to make this work in hardware.
  - Option #1: Have hardware set up to compare neighbouring bits at every position in  $\mathbb{A}$ , with adders in place for when the bits don't match.
    - Problem: This is a lot of hardware, which Booth's Algorithm is trying to avoid.
  - Option #2: Have hardware set up to compare two neighbouring bits, and have them move down through  $\mathbb{A}$ , looking for mismatched pairs.
    - Problem: Hardware doesn't move like that. Oops.

# Booth's Algorithm

- Still need to make this work in hardware...
  - Option #3: Have hardware set up to compare two neighbouring bits in the lowest position of  $A$ , and looking for mismatched pairs in  $A$  by shifting  $A$  to the right one bit at a time.
    - Solution! This could work, but the accumulated solution  $P$  would have to shift one bit at a time as well, so that when  $B$  is added or subtracted, it's from the correct position.

# Booth's Algorithm

*Note: unlike the accumulator, the bits here are being shifted to the right!*

- Steps in Booth's Algorithm:
  1. Designate the two multiplicands as A & B, and the result as some product P.
  2. Add an extra zero bit to the right-most side of A.
  3. Repeat the following for each original bit in A:
    - a) If the last two bits of A are the same, do nothing.
    - b) If the last two bits of A are 01, then add B to the highest bits of P.
    - c) If the last two bits of A are 10, then subtract B from the highest bits of P.
    - d) Perform one-digit arithmetic right-shift on both P and A.
  4. The result in P is the product of A and B.

# Booth's Algorithm Example

- Example:  $(-5) * 2$

- Steps #1 & #2:

- $A = -5 \rightarrow 11011$

- Add extra zero to the right  $\rightarrow A = 110110$

- $B = 2 \rightarrow 00010$

- $-B = -2 \rightarrow 11110$

- $P = 0 \rightarrow 00000\ 00000$

# Booth's Algorithm Example

- Step #3 (repeat 5 times):

- Check last two digits of A:

1101 10




- Since digits are 10, subtract B from the most significant digits of P:

P	00000	00000
-B	+11110	
P'	<u>11110</u>	00000

- Arithmetic shift P and A one bit to the right:

- A = 111011      P = 11111 00000

# Booth's Algorithm Example

- Step #3 (repeat 4 more times):
  - Check last two digits of A:  
1110 11 
  - Since digits are 11, do nothing to P.
  - Arithmetic shift P and A one bit to the right:
    - A = 111101    P = 11111 10000

# Booth's Algorithm Example

- Step #3 (repeat 3 more times):

- Check last two digits of A:

1111 01



- Since digits are 01, add B to the most significant digits of P:

P	11111	10000
+B	+00010	
P'	<u>00001</u>	<u>10000</u>

- Arithmetic shift P and A one bit to the right:

- A = 111110      P = 00000 11000

# Booth's Algorithm Example

- Step #3 (repeat 2 more times):

- Check last two digits of A:

1111 10



- Since digits are 10, subtract B from the most significant digits of P:

P	00000	11000
-B	+11110	
P'	<u>11110</u>	<u>11000</u>

- Arithmetic shift P and A one bit to the right:
  - A = 111111      P = 11111 01100



# Booth's Algorithm Example

- Step #3 (final time):
  - Check last two digits of A:  
 $1111 \boxed{11}$
  - Since digits are 11, do nothing to P:
  - Arithmetic shift P and A one bit to the right:
    - $A = 111111$      $P = 11111\ 10110$

- Final product:  $P = 111110110$   
 $= -10$